

Edexcel Physics IGCSE

Topic 2: Electricity

Summary Notes

(Content in bold is for physics only)



Mains electricity

Dangers of electricity

Hazards:

- **Damaged insulation** – contact with the wire due to gaps in the insulation can cause an **electric shock** or pose a **fire hazard** by creating a short circuit.
- **Overheating of cables** – high currents passing through thin wire conductors cause the wires to heat up to very high temperatures which could **melt the insulation** and cause a **fire**.
- Damp conditions – water can conduct a current so wet electrical equipment can cause an **electric shock**.

Fuses and circuit breakers:

- A **fuse** is a thin piece of **wire** which overheats and **melts** if the **current is too high, protecting the circuit**. They have a current **rating** which should be slightly higher than the current used by the device in the circuit. The most common are 3A, 5A and 13A.
- **Circuit breakers** consist of an automatic **electromagnet** switch which which **breaks the circuit** if the **current rises over a certain value**. This is better than a fuse as it can be **reset** and used again, and they operate **faster**.

Earthing metal cases:

- Earth wires create a **safe route** for current to flow through in the case of a **short circuit**, preventing electric shocks.
- Earth wires have a **very low resistance** so a strong current surges through them which breaks the fuse and disconnects the appliance.

Double insulation:

- Appliances with **double insulation** have either **plastic casings** or have been designed so that the earth wire **cannot touch** the metal casing, preventing them from giving an electric shock.

Electrical transfer of energy

Energy, measured in **joules (J)**, is transferred from **chemical** energy in the **battery** to **electrical** energy used by **circuit components** and then to the **surroundings**.

- The **power** of a component is measured in **watts (W)** and is given by $P=IV$ (by using $V=IR$, this can be shown to be equivalent to $P=I^2R$ and $P=V^2/R$). Using this equation, the energy transferred is given by $E=IVt$.

Alternating current and direct current

In a **direct current**, the current only flows in **one direction** whereas in an **alternating current**, the current continuously **changes direction**.

Mains electricity is an alternating current (a.c.) whereas the current supplied by a **cell or battery** is direct current (d.c.).



Energy and voltage in circuits

Current

Current I is measured in **amperes (A)** and is the **rate of flow of charge** at a **point** in the circuit.

- The current is given by $I=Q/t$, where Q is measured in **coulombs (C)** and t in **seconds (s)**.
- In metals, current is due to a **flow of electrons**. Because electrons are **negatively charged**, conventional current (which is the rate of flow of **positive charge**) is in the **opposite** direction to the flow of electrons.
- Current is **conserved** at a **junction** in a circuit because charge is always conserved.

Potential difference


Potential difference V is measured in **volts (V where $1\text{ V} = 1\text{ J C}^{-1}$)** and is the **work done per unit charge** in moving **between two points** in a circuit.

- The potential difference is given by $V=E/Q$.
- It is measured with a **voltmeter** placed in **parallel** across the component.
- The higher the potential difference, the greater the current.

Resistance

The **resistance** of a component is measured in **ohms (Ω)** and is given by the potential difference across it divided by the current through it, i.e. $R=V/I$. The greater the resistance, the harder it is for current to flow through the component.

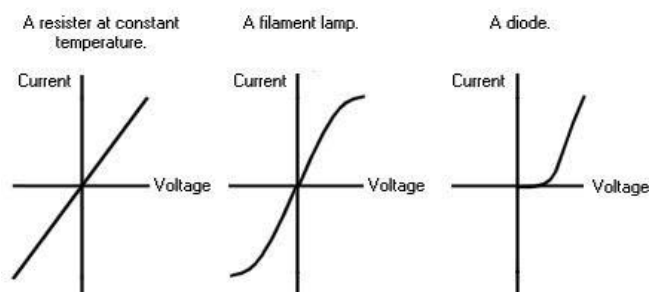In an **ohmic conductor** (such as a **resistor at a constant temperature**), the current is directly proportional to the voltage (i.e. it has constant resistance). In a non-ohmic conductor (such as a **filament lamp**), the resistance changes as the voltage and current changes.



In a filament lamp, this is because as the **current increases** through the filament, so does the **temperature**, which means **electrons and ions vibrate more** and **collide more**, increasing **resistance**.

A **thermistor** is a resistor whose resistance decreases as the **temperature** increases.

A **light dependent resistor** is a resistor whose resistance decreases as **light intensity** increases.

Electric circuits


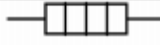



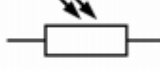
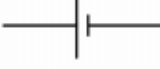

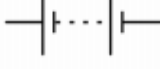

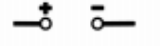
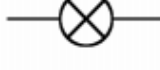
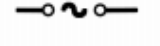



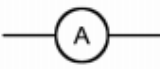

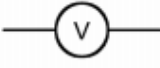
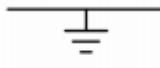

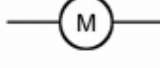
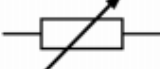
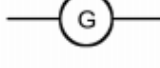

Series:

- Components are connected **end to end** in one loop
- The **same current** flows through every component
- The **potential difference is shared** across each component (i.e. the sum of the p.d.s across the components is equal to the total p.d. across the supply).
- The total resistance is the **sum of the resistances** of each component $R_T = R_1 + R_2 + \dots$



Parallel:

- Components are connected to the power supply in **separate branches**
- The **current is shared** between each branch (i.e. the sum of the currents in the separate branches is equal to the current through the source)
- The **potential difference** is the **same** across every branch
- Connecting lamps in parallel is advantageous because if one breaks, current can still pass through the rest.

Description	Symbol	Description	Symbol
Conductors crossing with no connection		Heater	
Junction of conductors		Thermistor	
Open switch		Light-dependent resistor (LDR)	
Cell		Diode	
Battery of cells		Light-emitting diode (LED)	
Power supply (DC)		Lamp	
Power supply (AC)		Loudspeaker	
Transformer		Microphone	
Ammeter		Electric bell	
Voltmeter		Earth or ground	
Fixed resistor		Motor	
Variable resistor		Generator	
		Fuse/circuit breaker	



Electric charge

Charge is measured in coulombs. There are **positive** and **negative** charges; **unlike** charges **attract** and **like** charges **repel**.

- Charging a body involves the **addition** or **removal** of **electrons**.
- **Conductors** such as **metals** allow electrons to flow through them whereas **insulators** such as **plastics** impede the flow of electrons.
 - When two insulators are **rubbed** together, electrons move from one to the other and they become charged. For example, when a **rod** is rubbed with a **cloth**, electrons are transferred from the rod onto the cloth and the rod becomes positively charged.

Electrostatic phenomena caused by the movement of electrons have many useful applications but also pose many risks.

- Dangers of electrostatic charges include:
 - When **fuelling aircraft and tankers**, if enough charge builds up it can create a **spark**, igniting fuel and causing a **fire or explosion**. A wire can be attached so that the charge instead flows into the earth.
- Uses of electrostatic charges include:
 - In an **inkjet printer**, droplets of **ink** are **charged** and pass between **two charged metal plates**, one of which has a positive charge and the other a negative charge. The droplets are attracted to the plate with the opposite charge and repelled by the plate which the same charge and **deflected** towards a specific place on the paper.
 - In a **photocopier**, the image of a document is projected onto a **positively charged plate**; where light falls onto the plate, the charge leaks away. **Negatively charged toner particles** are attracted to the remaining positive areas. Paper is then placed over the plate and the toner is transferred to it, making the photocopy.

